



University of British Columbia  
Electrical and Computer Engineering  
ELEC291/ELEC292

## Project 2: Magnetic Field Controlled Robot.

Dr. Jesús Calviño-Fraga P.Eng.  
Department of Electrical and Computer Engineering, UBC  
Office: KAIS 3024  
E-mail: [jesusc@ece.ubc.ca](mailto:jesusc@ece.ubc.ca)  
Phone: (604)-827-5387

March 16, 2018

Project 2 Description

Copyright © 2012-2018, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

1

## Requirements

- Microcontroller Systems (two needed!):
  - One for the robot (the receiver). Receives commands and moves the robot around.
  - One for the Transmitter . It generates the magnetic field and sends commands to the Robot.
- Microcontroller Systems must be from different families.
- Programmed in C.
- The robot must be battery powered.
- Discrete MOSFET drivers.
- Commands transmitted to the robot from the transmitter:
  - **Stop.**
  - **Turn left.**
  - **Turn right.**
  - **Move Forward.**
  - **Move Backward.**
- Minimum range of 100 cm.
- **Task:** move three objects (200 cm<sup>3</sup>) from 'send' area to 'receive' area. Two 20cm circles 100cm apart.
- **Communication between robot and transmitter:** only magnetic field allowed. No Bluetooth, WIFI, radios, etc.

Project 2 Description

Copyright © 2012-2018, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

2

## Getting Started with a New Microcontroller System

1. Obtain/assemble the hardware. Also documentation: datasheets & manuals.
2. Obtain/install the development environment. Also documentation like manuals.
3. Obtain/install a means of putting the 'firmware' in the hardware. May require additional hardware tools and software.
4. Settle a workflow. Also: examples, application notes, and forums.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

3

## Getting Started with a New Microcontroller System


- In this course is not too difficult. Instructions provided for:
  - STM32F052: LQFP32. 64k flash. ST Microelectronics. ARM architecture.
  - LPC824: TSOP 20. 32k flash. NXP. ARM architecture.
  - PIC32MX130: DIP-28. 64k flash. Microchip. MIPS architecture.
  - ATmega328p: DIP-28. 32k flash. Atmel/Microchip. AVR architecture.
  - MSP430G2553. DIP-20. 16k flash. Texas Instruments. MSP430 architecture.
  - AT89LP51RC2. DIP-40. 32k flash. Atmel/Microchip. 8051 architecture. Used in first half of the course. Extra 'Makefile' examples in Connect.
  - EFM8 board with EFM8LB1. 64k flash. LQFP32. Silicon Labs. 8051 architecture. Used in second half of the course. Extra 'Makefile' examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

4
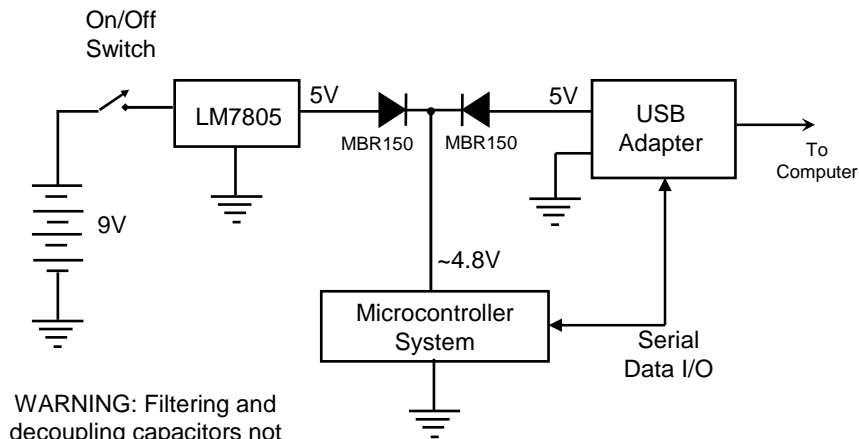
## Using Batteries to Power the Microcontroller System



WARNING: Filtering and decoupling capacitors not shown. Check LM7805 datasheet!

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

5

## The STM32F051 Microcontroller System

1. Hardware: Bare IC + Adapter in breadboard.
2. Development environment: GCC for ARM.
3. Flash Loader: Port of official FLASHER-STM32 from ST Microelectronics via BO23XS board.
4. Workflow: via Makefiles in CrossIDE. Examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


6

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

| Qty  | Supplier's#         | Man's #          | Description                      | Price |
|------|---------------------|------------------|----------------------------------|-------|
| 2    | BC1148CT-ND         | K104215Y5VE5TL2  | CAP CER 0.1UF 25V Y5V RADIAL     | 0.54  |
| 2    | BC1157CT-ND         | K105220Y5VE5TH5  | CAP CER 1UF 25V Y5V RADIAL       | 0.94  |
| 2    | 270QBK-ND           | CFR-25JB-52-270R | RES 270 OHM 1/4W 5% AXIAL        | 0.30  |
| 1    | 330QBK-ND           | CFR-25JB-52-330R | RES 330 OHM 1/4W 5% AXIAL        | 0.15  |
| 1    | 67-1102-ND          | SSL-LX5093HD     | LED RED DIFF 5MM ROUND T/H       | 0.55  |
| 1    | 67-1108-ND          | SSL-LX5093LGD    | LED GRN DIFF 5MM ROUND T/H       | 0.62  |
| 1    | MCP1700-3302E/TO-ND | MCP1700-3302E/TO | IC REG LDO 3.3V 0.25A TO92-3     | 0.57  |
| 1    | 497-13626-ND        | STM32F051K8T6    | IC MCU 32BIT 64KB FLASH 32LQFP   | 4.14  |
| 0.33 | 1528-1065-ND        | 1163             | SMT ADAPTERS 3 PACK 32QFN/TOFP   | 2.82  |
| 2    | A26509-16-ND        | 4-103741-0-16    | CONN HEADR BRKWAY .100 16POS STR | 3.12  |
| 2    | P8070SCT-ND         | EVQ-11A04M       | SWITCH TACTILE SPST-NO 0.02A 15V | 0.70  |

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The STM32F051 Microcontroller System

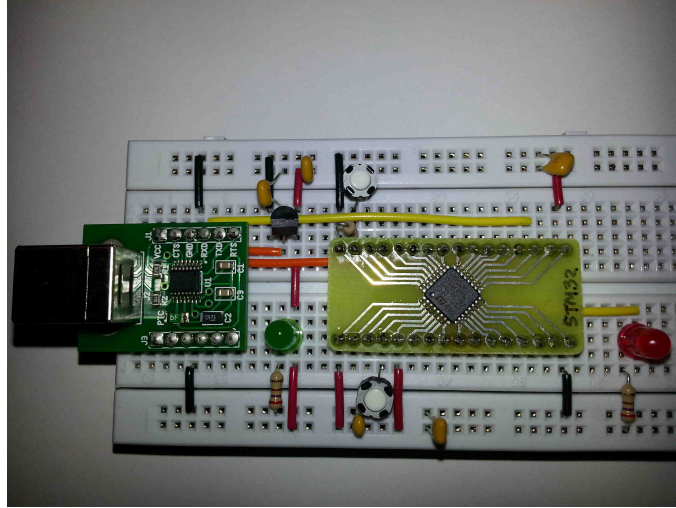

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

9

## The LPC824 Microcontroller System


1. Hardware: Bare IC + Adapter in breadboard.
2. Development environment: GCC for ARM.
3. Flash Loader: Port of lpc21isp via BO23XS board.
4. Workflow: via makefiles in CrossIDE. Examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

10

## The LPC824 Microcontroller System

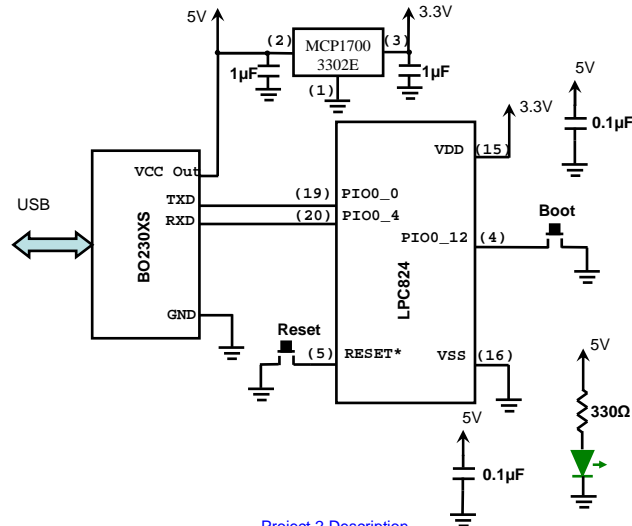

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

11

## The LPC824 Microcontroller System

| Qty  | Supplier's#         | Man's #          | Description                      | Price |
|------|---------------------|------------------|----------------------------------|-------|
| 2    | BC1148CT-ND         | K104Z15Y5VE5TL2  | CAP CER 0.1UF 25V Y5V RADIAL     | 0.54  |
| 2    | BC1157CT-ND         | K105Z20Y5VE5TH5  | CAP CER 1UF 25V Y5V RADIAL       | 0.94  |
| 1    | 1.0QBK-ND           | CFR-25JB-52-1R   | RES 1 OHM 1/4W 5% AXIAL          | 0.15  |
| 1    | 330QBK-ND           | CFR-25JB-52-330R | RES 330 OHM 1/4W 5% AXIAL        | 0.15  |
| 1    | 67-1102-ND          | SSL-LX5093HD     | LED RED DIFF 5MM ROUND T/H       | 0.55  |
| 1    | 67-1108-ND          | SSL-LX5093LGD    | LED GRN DIFF 5MM ROUND T/H       | 0.62  |
| 1    | MCP1700-3302E/TO-ND | MCP1700-3302E/TO | IC REG LDO 3.3V 0.25A TO92-3     | 0.57  |
| 1    | 568-11619-1-ND      | LPC824M201JDH20J | IC MCU 32BIT 32KB FLASH 20TSSOP  | 2.74  |
| 0.33 | 1528-1066-ND        | 1206             | SMT ADAPTERS 3 PACK 20SOIC/TSSOP | 2.13  |
| 2    | A26509-10-ND        | 4-103741-0-10    | CONN HEADR BRKWAY .100 10POS STR | 2.32  |
| 2    | P8070SCT-ND         | EVQ-11A04M       | SWITCH TACTILE SPST-NO 0.02A 15V | 0.70  |


Total 10.71

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

12

## The LPC824 Microcontroller System

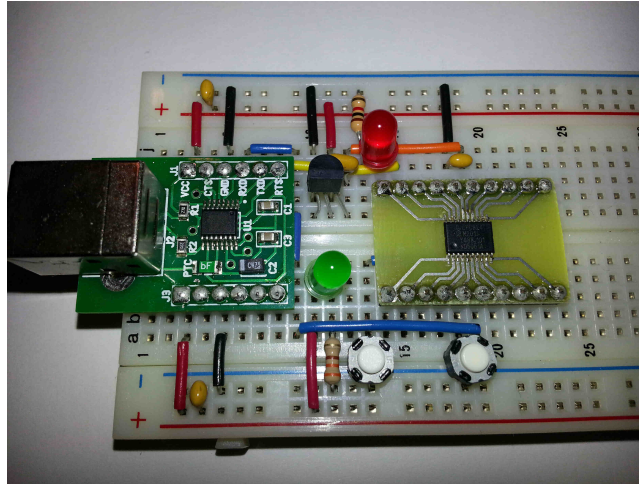

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

13

## The PIC32 Microcontroller System


1. Hardware: Bare IC in breadboard.
2. Development environment: XC32 from Microchip. (Derived from GCC but...)
3. Flash Loader: Pro32 via BO230XS board by yours truly.
4. Workflow: via Makefiles in CrossIDE. Examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

14

## The PIC32 Microcontroller System

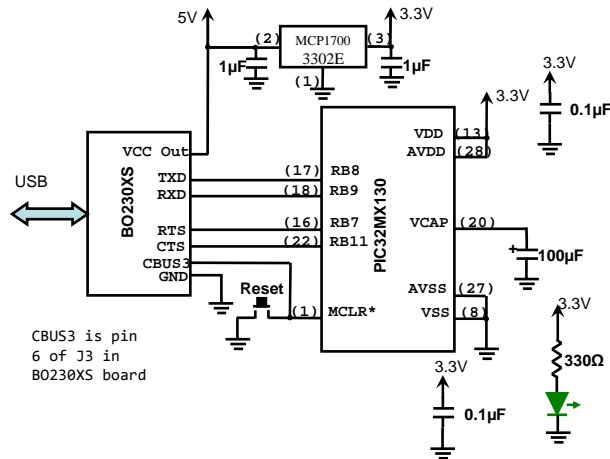

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

15

## The PIC32 Microcontroller System

| Qty | Supplier's #            | Man's #              | Description                      | Price |
|-----|-------------------------|----------------------|----------------------------------|-------|
| 2   | BC1148CT-ND             | K104Z15Y5VE5TL2      | CAP CER 0.1UF 25V Y5V RADIAL     | 0.54  |
| 2   | BC1157CT-ND             | K105Z20Y5VE5TH5      | CAP CER 1UF 25V Y5V RADIAL       | 0.94  |
| 2   | 330QBK-ND               | CFR-25JB-52-330R     | RES 330 OHM 1/4W 5% AXIAL        | 0.30  |
| 1   | 67-1102-ND              | SSL-LX5093HD         | LED RED DIFF 5MM ROUND T/H       | 0.55  |
| 1   | 67-1108-ND              | SSL-LX5093LGD        | LED GRN DIFF 5MM ROUND T/H       | 0.62  |
| 1   | MCP1700-3302E/TO-ND     | MCP1700-3302E/TO     | IC REG LDO 3.3V 0.25A TO92-3     | 0.57  |
| 1   | PIC32MX130F064B-I/SP-ND | PIC32MX130F064B-I/SP | IC MCU 32BIT 64KB FLASH 28SDIP   | 4.23  |
| 1   | 493-1548-ND             | UHE1E101MED          | CAP ALUM 100UF 20% 25V RADIAL    | 0.41  |
| 2   | P8070SCT-ND             | EVQ-11A04M           | SWITCH TACTILE SPST-NO 0.02A 15V | 0.70  |

Total 8.86


Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

16



## The PIC32 Microcontroller System

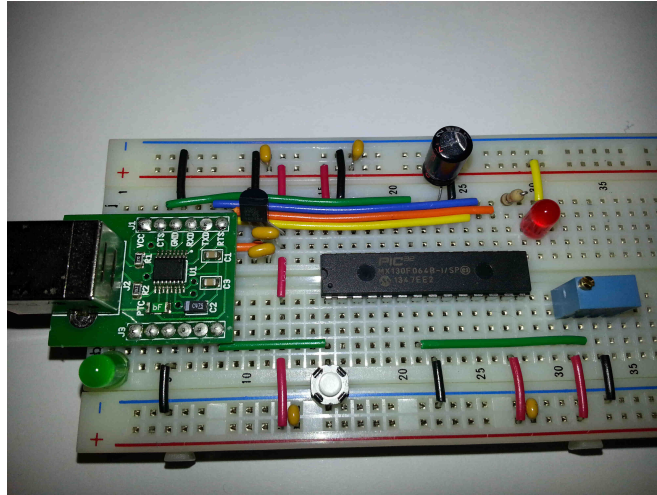

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

17

## The AVR Microcontroller System


1. Hardware: Bare IC in breadboard.
2. Development environment: Atmel AVR 8-bit Toolchain for Windows.
3. Flash Loader: spi\_atmega328 via BO230XS board by yours truly.
4. Workflow: via Makefiles in CrossIDE. Examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

18

# The AVR Microcontroller System

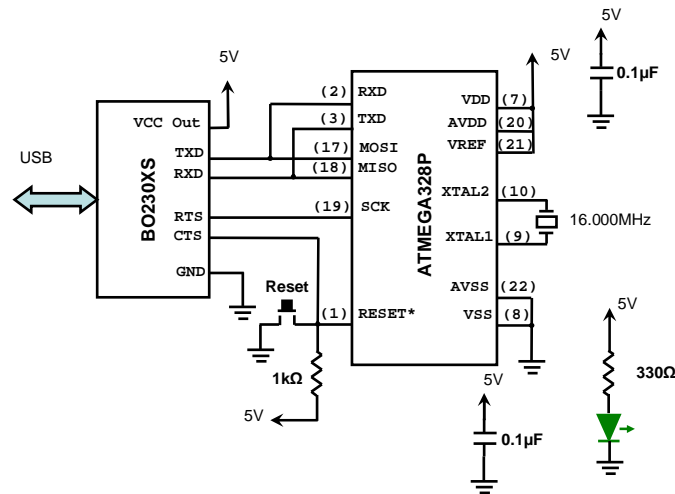

## Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

19

# The AVR Microcontroller System

| Qty | Supplier's#      | Man's #          | Description                      | Price |
|-----|------------------|------------------|----------------------------------|-------|
| 3   | BC1148CT-ND      | K104Z15Y5VE5TL2  | CAP CER 0.1UF 25V Y5V RADIAL     | 0.81  |
| 1   | 1.0KQBK-ND       | CFR-25JB-52-1K   | RES 1K OHM 1/4W 5% AXIAL         | 0.15  |
| 2   | 330QBK-ND        | CFR-25JB-52-330R | RES 330 OHM 1/4W 5% AXIAL        | 0.30  |
| 1   | 67-1102-ND       | SSL-LX5093HD     | LED RED DIFF 5MM ROUND T/H       | 0.55  |
| 1   | 67-1108-ND       | SSL-LX5093LGD    | LED GRN DIFF 5MM ROUND T/H       | 0.62  |
| 1   | CTX1085-ND       | ATS16B           | CRYSTAL 16.000MHZ 18PF T/H       | 0.54  |
| 1   | ATMEGA328P-PU-ND | ATMEGA328P-PU    | IC MCU 8BIT 32KB FLASH 28DIP     | 3.24  |
| 1   | P8070SCT-ND      | EVQ-11A04M       | SWITCH TACTILE SPST-NO 0.02A 15V | 0.35  |


Total 6.56

## Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

20

## The AVR Microcontroller System

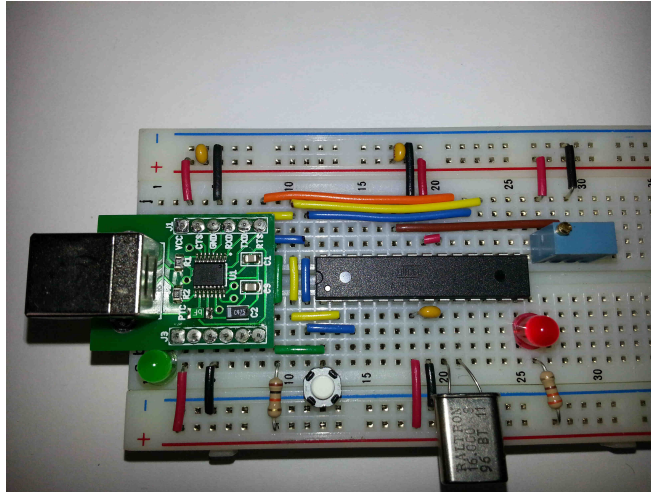

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

21

## The MSP430 Microcontroller System


1. Hardware: Bare IC + Adapter in breadboard.
2. Development environment: GCC for MSP430.
3. Flash Loader: MSP430\_prog via BO23XS board by yours truly.
4. Workflow: via makefiles in CrossIDE. Examples in Connect.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

22

## The MSP430 Microcontroller System

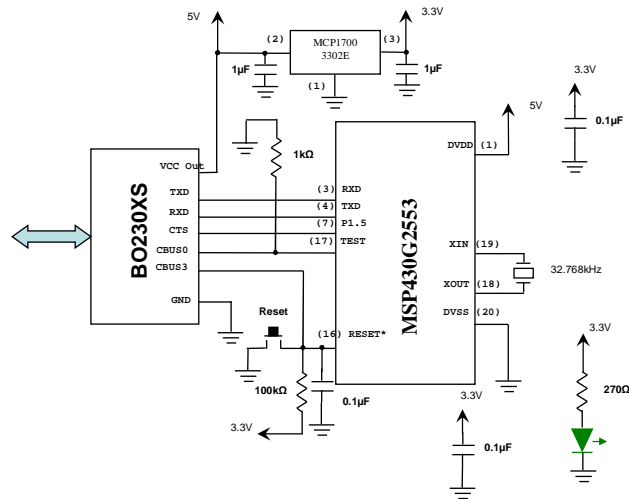

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

23

## The MSP430 Microcontroller System

| Quantity | Digi-Key Part #     | Description                     |      |
|----------|---------------------|---------------------------------|------|
| 3        | BC1148CT-ND         | 0.1uF ceramic capacitors        | 0.73 |
| 2        | BC1157CT-ND         | 1uF ceramic capacitor           | 0.90 |
| 2        | 270QBK-ND           | 270Ω resistor                   | 0.30 |
| 1        | 1.0KQBK-ND          | 1kΩ resistor                    | 0.15 |
| 1        | 100KQBK-ND          | 100kΩ resistor                  | 0.15 |
| 1        | MCP1700-3302E/TO-ND | IC REG LINEAR 3.3V 250MA TO92-3 | 0.57 |
| 1        | 67-1108-ND          | LED 5MM GREEN                   | 0.59 |
| 1        | 300-8842-ND         | CRYSTAL 32.7680KHZ 7PF T/H      | 0.35 |
| 1        | 296-28429-5-ND      | MSP430G2553                     | 3.93 |
| 1        | P8070SCT-ND         | Push button switch              | 0.34 |


\$8.01

24

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The MSP430 Microcontroller System

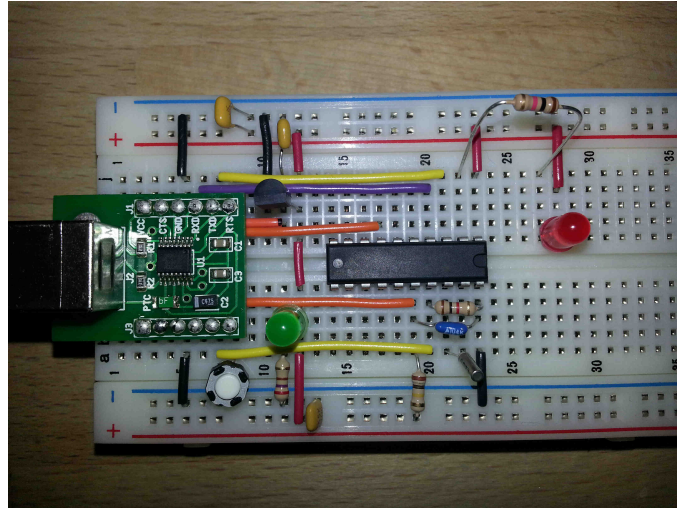


Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

25

## Magnetic Field Controlled Robot

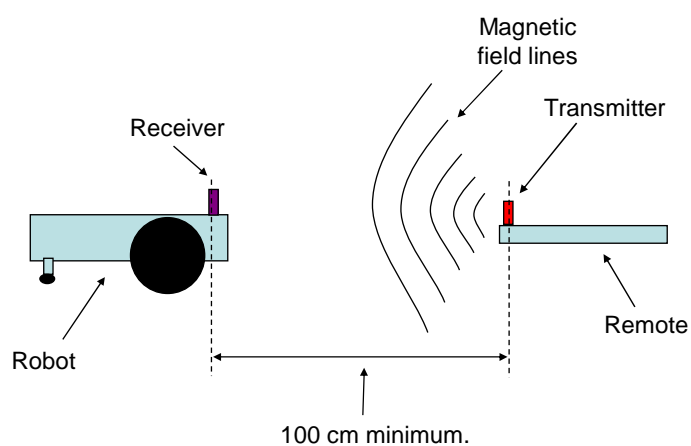

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

26

## Transmitter


- It is a series RLC circuit you should know from ELEC202.
- The inductor (L) is provided in the robot kit. You can use any inductor you want!
- For the capacitor (C) you can use the capacitors you already have, but they may not work very well. Optionally you can buy a much better capacitor in local electronics parts stores.
- You need a safe, stable, and reliable transmitter for your project.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

27

## Simplified RLC Transmitter Circuit

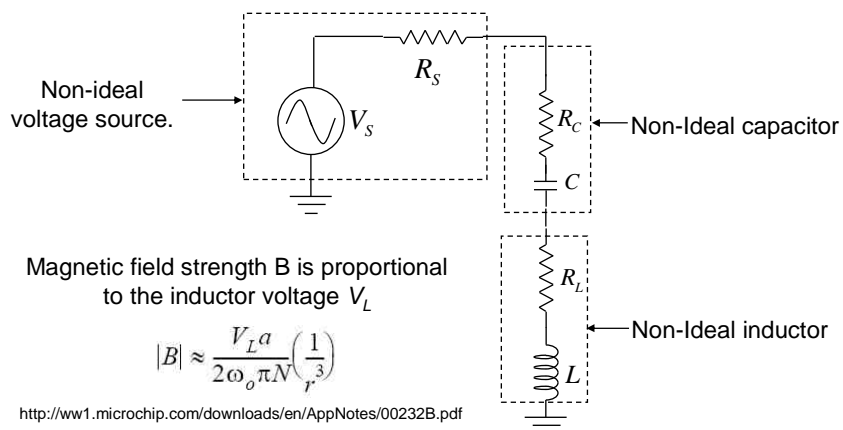


Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

28

## Simplified RLC Transmitter Circuit

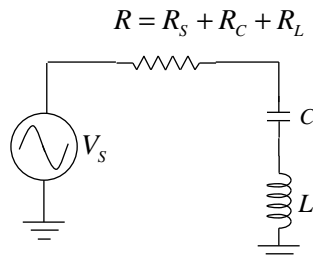

For maximum voltage at the inductor, the circuit must be tuned:

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$


Other factors affect the magnitude of  $V_L$ . Use phasor analysis!

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

29

## Simplified RLC Transmitter Circuit

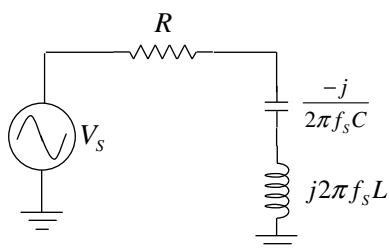

$$i = \frac{V_s}{R - \frac{j}{2\pi f_s C} + j2\pi f_s L} = \frac{V_s}{R}$$

At the tuned frequency this two values are equal!

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$


$$V_L = \frac{jV_s 2\pi f_s L}{R}$$

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

30
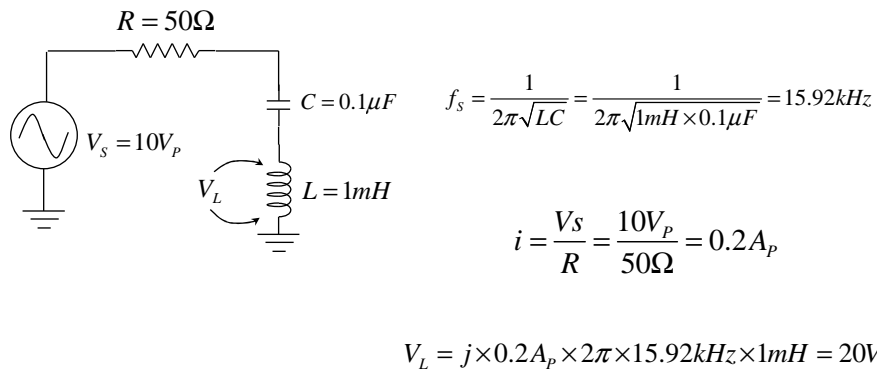
## Simplified RLC Transmitter Circuit test using function generator.




Not good enough. You'll need about 150 V<sub>p</sub>!

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

31
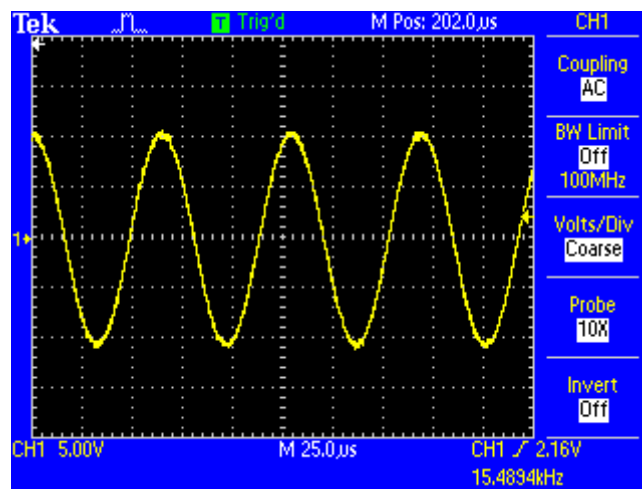
## V<sub>S</sub> Using a Function Generator




Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

32



## $V_L$ From the Circuit Above

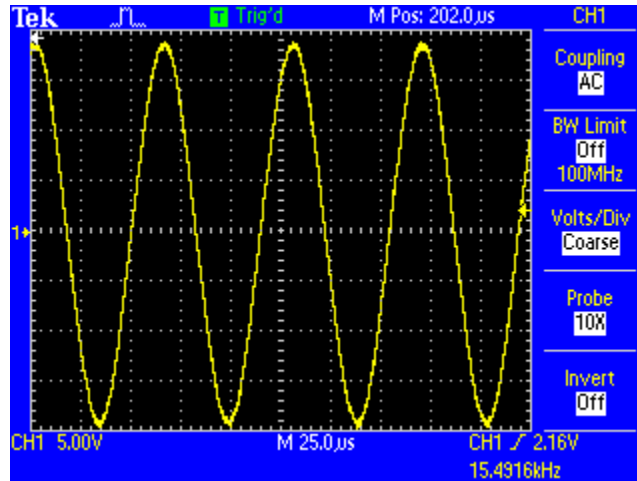

Project 2 Description  
Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

33

## Maximizing $V_L$

- Increase  $V_S$ .
  - Con: Large source voltages are difficult to handle. Potentially dangerous.
- ~~Increase  $f_s$ .~~
  - Con: It won't work because  $f_s$  is in the denominator of the magnetic field strength equation.
- ~~Increase  $L$ .~~
  - Con: you'll need to get new inductors. The ones you have are pretty good! Is it also in the magnetic field strength equation?!
- Decrease  $R$ .
  - Con: None! Decrease  $R$ !

$$|B| \approx \frac{V_L a}{2\omega_0 \pi N} \left( \frac{1}{r^3} \right)$$

Project 2 Description  
Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

34

$V_s$

- It can be an square wave!
- The Fourier Series of a square wave is given by:

$$x(t) = \frac{4}{\pi} \sum_{k=1}^{\infty} \frac{\sin(2\pi(2k-1)ft)}{2k-1} = \frac{4}{\pi} \left( \sin(2\pi ft) + \frac{1}{3} \sin(6\pi ft) + \frac{1}{5} \sin(10\pi ft) + \dots \right)$$

Fundamental
3<sup>rd</sup> harmonic
5<sup>th</sup> harmonic

**Bonus: The amplitude of the fundamental is  $4/\pi=1.273$  times the amplitude of the square wave!**


Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

35

$V_s$ : use an H-bridge!

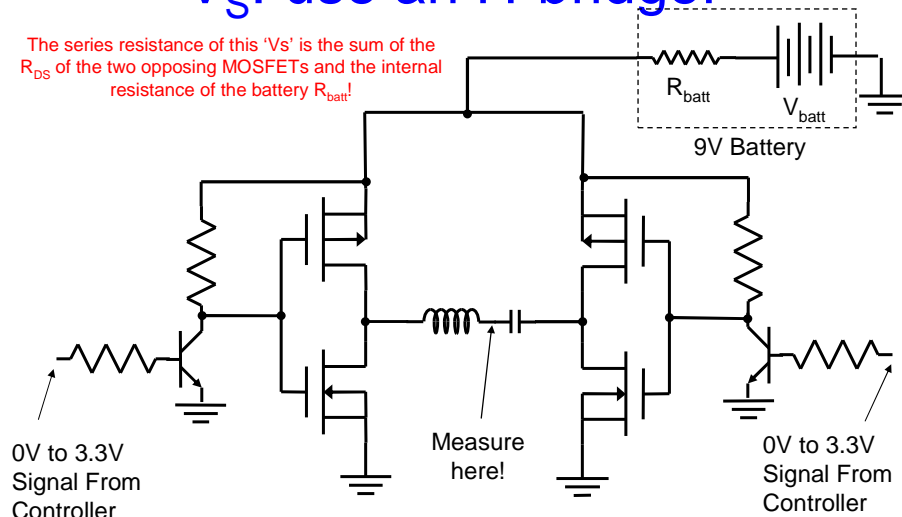The series resistance of this ' $V_s$ ' is the sum of the  $R_{DS}$  of the two opposing MOSFETs and the internal resistance of the battery  $R_{batt}$ !



Optocouplers are not fast enough for transmitter frequency! Using BJTs instead.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

36

## Finding the Tuned Frequency

- At the tuned frequency the output voltage as indicated in the previous slide is at its maximum: 100s of volts! (I've seen up to 800V! 200V is more common.)
- Use the oscilloscope to CAREFULLY check the signal. The maximum voltage the oscilloscope can take is 300V. Therefore you must use an oscilloscope probe with 10x attenuation.
- Use the program 'freq\_gen.c' available in connect to find the tuned frequency.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

37

## WARNING!

- If you use a low resistance source, like the H-bridge from the previous slides, the peak voltage at both the inductor and capacitor may increase to hundreds of volts:
  - If you touch the circuit you will get shocked! **DO NOT TOUCH THE INDUCTOR/CAPACITOR** when the circuit is on. Safety tip: use a smaller voltage (<100Vp) for development and test. When design/test is done increase the voltage to its maximum.
  - The capacitor must be rated for the generated voltage. Putting a 50V capacitor into a 300V circuit may result in a blown capacitor and/or weak magnetic field.
  - Connect instruments to the circuit that work at the rated voltage.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


38

## The Inductor

- DigiKey part number M8275-ND

Don't drop the inductor.  
The ferrite core may  
break!

|                        |           |
|------------------------|-----------|
| <b>Type</b>            | Wirewound |
| <b>Material - Core</b> | Ferrite   |
| <b>Inductance</b>      | 1mH       |
| <b>Tolerance</b>       | ±20%      |
| <b>Current Rating</b>  | 1A        |
| <b>DC Resistance</b>   | 0.55 Ohms |

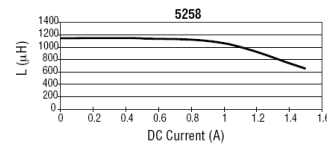

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

39

## The Capacitor


- The peak value of the voltage across the capacitor is equal to the peak value across the inductor. The capacitor **MUST** be rated for the operating voltage! If not:
  - The capacitor may over heat and explode.
  - The capacitor may short circuit and catch fire.
  - The capacitor may introduce too much series resistance.
- Go to RP, Main, or Lee's and buy a good capacitor!

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

40

## The Receiver

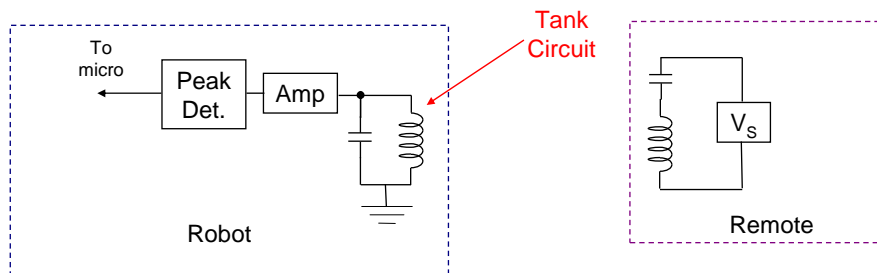

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

41

## Receiving/Transmit Commands Using the Magnetic Field

- Using Extra Uart (a form of AM):
  - For example: assume "field present" is logic one.
  - Connect the output of the comparator (don't forget the pull-up resistor) to the receive pin of UART1. (More on this later)
- PWM of magnetic field:
  - Different pulse widths correspond to different commands.
- FM of magnetic field:
  - Different, but close frequencies correspond to different commands.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

42

## Robot Construction

| Part #                 | Description                                       |
|------------------------|---|
| Solarbotics GM4        | Gear Motor 4 - Clear Servo                        |
| Lynxmotion Servo Wheel | 2.63" x 0.35" (pair) wheels                       |
| Tamiya 70144           | Ball Caster                                       |
| 4 x AA                 | Battery holder                                    |
| 1 x 9V cable           | 9V battery clip                                   |
| Unfolded chassis       | Aluminum chassis made using the water jet cutter. |

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

43

## Fitting the Wheels to the Motors

### Question:

*"We're finally assembling our rover and the wheels seem to not have the same spline pattern as the motor shaft. I'd rather not force these to mate. Is this unusual? Can you suggest a solution?"*

### Answer:

The wheels pressure fit into the motor shafts. The wheels are flexible so they will expand a bit making an excellent and tight fit to the shaft. It is hard to press the wheels into the shafts, but if you used the provided screws, you can fit them very easily by screwing them in.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

44

## Sending Commands From the Remote to the Robot


- Check application note from Microchip. It describes On-Off Keying for data transmission:  
<http://ww1.microchip.com/downloads/en/AppNotes/00232B.pdf>
- A minimum of five commands required:
  - **Move Left.**
  - **Move Right.**
  - **Move Forward.**
  - **Move Backward.**
  - **Stop.**
- Use buttons, PuTTY, nunchuck, joystick, etc. to select commands.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

45

## Data Bit Rise and Fall Times

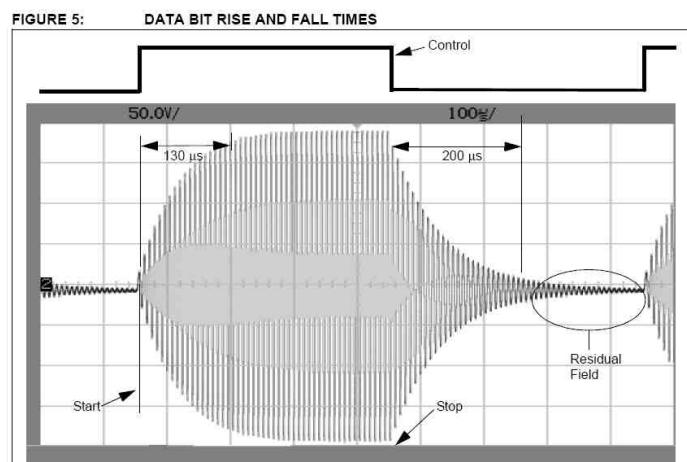


Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

46

## Data Modulation Formats

FIGURE 6: DATA MODULATION FORMATS

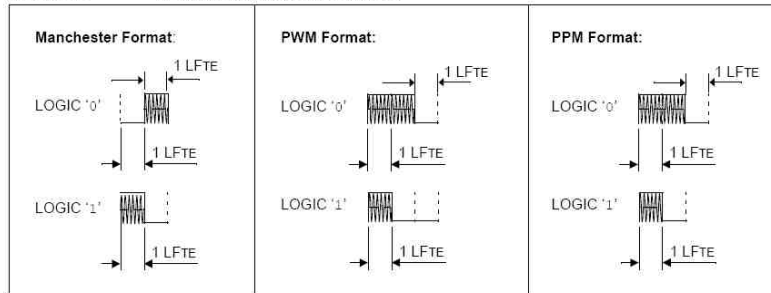

Since you'll need to transmit only a few data bits, it is not a problem to assume 'field present' equal 'logic one' and 'field not present' equal 'logic zero'. The baud rate has to be very low.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

47

## Use EFM8 second UART!

- The EFM8LB1 comes with two UARTs:
  - UART0: is the standard serial port that comes with most 8051 compatible microcontrollers.
  - UART1: is an enhanced UART available in many Silabs microcontrollers. Example posted in Connect.
- To modulate the magnetic field, you can use UART1 at a very low baud rate. 110 baud worked for me. The faster the better!

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

48



## C programmed.

- Both the robot and the remote must be programmed using the C programming language.
- You may 'inline' small portions of assembly code, but the bulk of your code must be C.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

49

## Battery powered.

- Your project must be battery powered. This includes the electronics and motors of both the transmitter and receiver
- A 9 volt battery strap and a 4 x AA battery holder are included in the parts kit for this project.
- You can use any kind of batteries you want, provided that you acquire the batteries and the holders yourself.
- WARNING: batteries are neither included in the parts kits nor they will be provided in the lab. You must buy your own batteries.
- Brand name batteries have lower internal resistance, but they are more expensive.

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

50

**WARNING!**  
**HIGH VOLTAGE CIRCUIT. DO**  
**NOT TOUCH. HANDLE WITH**  
**EXTREME CARE.**

Extra requirement:  
Add this sign to your  
transmitter. →



Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or  
revised without explicit written permission from the copyright owner.

51

## Project 2 Due Dates

Function demo: March 28/29

Report: April 6

Project 2 Description

Copyright © 2012-2018, Jesus Calvino-Fraga. Not to be copied, used, or  
revised without explicit written permission from the copyright owner.

52